

Bilkent University EEE102

Lab 04 Report:

Arithmetic Logic Unit

Burak Gökkaya 22202209

Purpose:

The aim of this lab was to build an Arithmetic Logic Unit (ALU). It should have 8 functions including at least one bitwise, one shift, addition and subtraction operators.

Methodology:

Firstly we understood what is ALU. Then we decided which functions we will use. I choose:

- Adder (OP is '000')
- Subtractor (OP is '001')
- NAND (OP is '010')
- Comparator (OP is '011')
- XOR (OP is '100')
- Rotation (OP is '101')
- Shifting Left (OP is '110')
- Shifting Right (OP is '111')

Then I started to write the functions one by one. For example, for adder I used half adders and full adders. Then I generated the RTL schematic of my code.

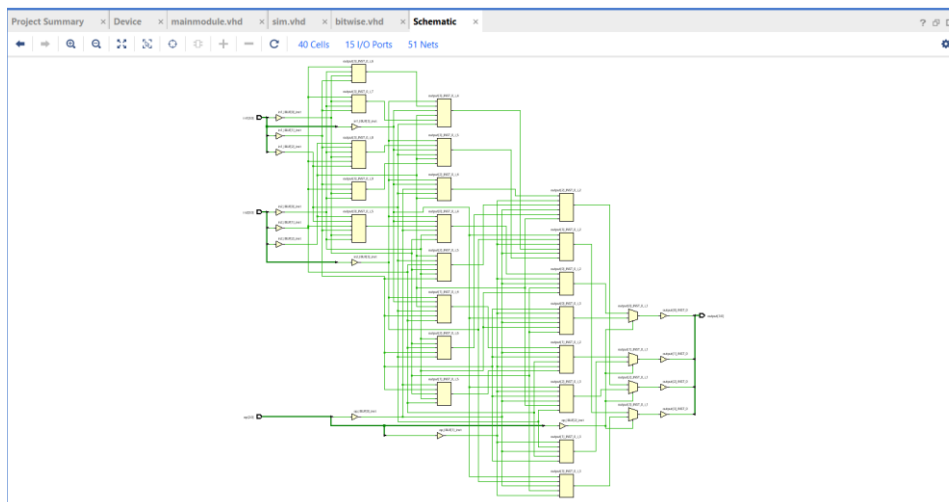


Figure 1: Schematic of system

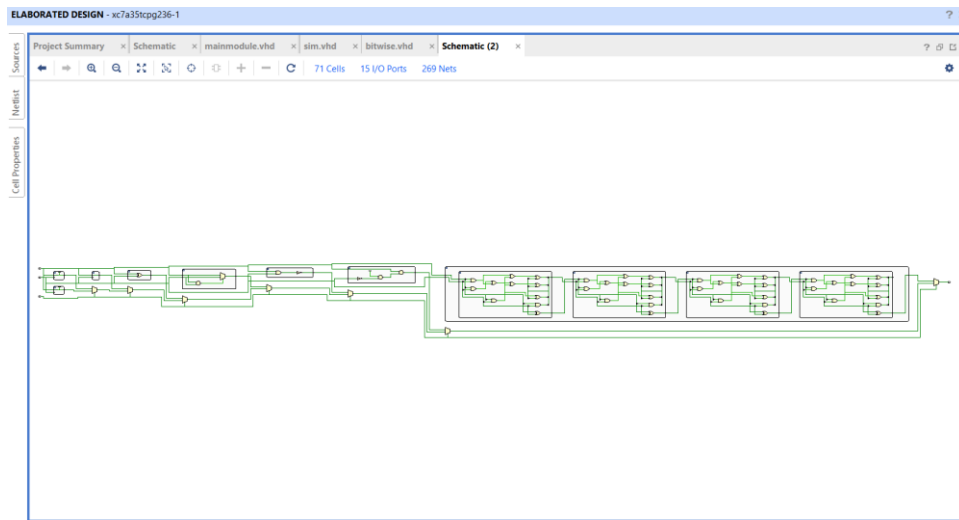


Figure 2: Elaborated Design

After that we simulated the code and it worked like what I wanted.

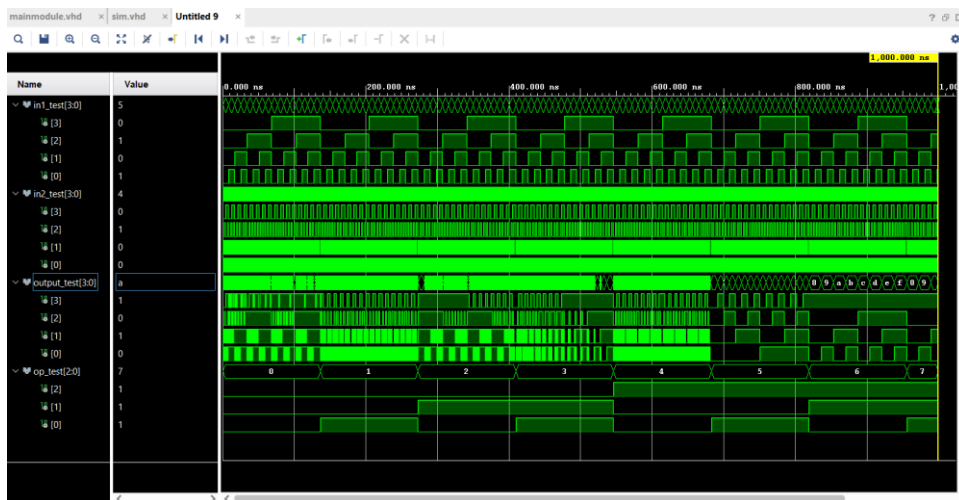


Figure 3: Simulation of code (op is select input)

After all of these stages, I generated bitstream and implemented the code on BASYS3.

 


Figure 4: Shifting right to 0111

 


Figure 5: Addition of '0110' and '0110'

 


Figure 6: Subtraction of '0110' and '0110'

Conclusion:

As a result, I understood BASYS3 mechanism very good and I learned ALU. IN this lab we wrote some functions and it helps us for understanding computer algorithm. So that it was really successfull experiment.

Appendix:

----main module

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity mainmodule is

Port (in1 : in STD_LOGIC_VECTOR (3 downto 0);

in2 : in STD_LOGIC_VECTOR (3 downto 0);

op : in STD_LOGIC_VECTOR (2 downto 0);

output : out STD_LOGIC_VECTOR (3 downto 0));

end mainmodule;

architecture Behavioral of mainmodule is

component adder is

Port (A : in STD_LOGIC_VECTOR (3 downto 0);

B : in STD_LOGIC_VECTOR (3 downto 0);

Sum : out STD_LOGIC_VECTOR (3 downto 0);

Cout : out STD_LOGIC_VECTOR (3 downto 0));

end component;

component subt is

Port (A : in STD_LOGIC_VECTOR(3 downto 0);

B : in STD_LOGIC_VECTOR(3 downto 0);

diff : out STD_LOGIC_VECTOR(3 downto 0));

end component;

component shiftRight is

Port (A : in STD_LOGIC_VECTOR(3 downto 0);

B : in STD_LOGIC_VECTOR(3 downto 0);

resR : out STD_LOGIC_VECTOR(3 downto 0));

end component;

component shiftLeft is

```
Port ( A : in STD_LOGIC_VECTOR(3 downto 0);  
      B : in STD_LOGIC_VECTOR(3 downto 0);  
      resL : out STD_LOGIC_VECTOR(3 downto 0));
```

end component;

component comparison is

```
Port ( A : in STD_LOGIC_VECTOR(3 downto 0);  
      B : in STD_LOGIC_VECTOR(3 downto 0);  
      comp : out STD_LOGIC_VECTOR(3 downto 0));
```

end component;

component Bitwise_Logic is

```
Port ( A : in STD_LOGIC_VECTOR(3 downto 0);  
      B : in STD_LOGIC_VECTOR(3 downto 0);  
      Result : out STD_LOGIC_VECTOR(3 downto 0));
```

end component;

component rotate is

```
Port ( A : in STD_LOGIC_VECTOR(3 downto 0);  
      B : in STD_LOGIC_VECTOR(3 downto 0);  
      resRo : out STD_LOGIC_VECTOR(3 downto 0));
```

end component;

component bitwise_nand is

```
Port ( A : in STD_LOGIC_VECTOR(3 downto 0);  
      B : in STD_LOGIC_VECTOR(3 downto 0);  
      Result_nand : out STD_LOGIC_VECTOR(3 downto 0));
```

end component;

signal temp_result,out1,out2,out3,out4,out5,out6,out7,out8 : STD_LOGIC_VECTOR(3 downto 0);

begin

u1: adder

port map(A => in1, B => in2, Sum => out1);

```

u2: subtr
port map(A => in1, B => in2, diff => out2);

u3: bitwise_nand
port map(A => in1, B => in2, Result_nand => out3);

u4: comparison
port map(A => in1, B => in2, comp => out4);

u5: Bitwise_Logic
port map(A => in1, B => in2, Result => out5);

u6: rotate
port map(A => in1, B => in2, resRo => out6);

u7: shiftLeft
port map(A => in1, B => in2, resL => out7);

u8: shiftRight
port map(A => in1, B => in2, resR => out8);

process(op, out1, out2, out3, out4, out5, out6, out7, out8)
begin
    if op = "000" then
        output <= out1;
    elsif op = "001" then
        output <= out2;
    elsif op = "010" then
        output <= out3;
    elsif op = "011" then
        output <= out4;
    elsif op = "100" then
        output <= out5;
    elsif op = "101" then
        output <= out6;
    elsif op = "110" then
        output <= out7;
    else

```

```

        output <= out8;
    end if;
end process;
end Behavioral;

```

-----full adder

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

entity adder is

```

    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          Sum : out STD_LOGIC_VECTOR (3 downto 0);
          Cout : out STD_LOGIC_VECTOR (3 downto 0));

```

end adder;

architecture Behavioral of adder is

```

    signal sumHA1, sumHA2, carryHA1, carryHA2, sumHA3, carryHA3, sumHA4, carryHA4 :
    STD_LOGIC_VECTOR (3 downto 0);

```

component halfadder is

```

    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          sum : out STD_LOGIC_VECTOR (3 downto 0);
          carry : out STD_LOGIC_VECTOR (3 downto 0));

```

end component;

begin

-- First half adder

```

HA1: halfadder port map (A => A, B => B, sum => sumHA1, carry => carryHA1);
HA2: halfadder port map (A => sumHA1, B => carryHA1, sum => sumHA2, carry => carryHA2);
HA3: halfadder port map (A => sumHA2, B => carryHA2, sum => sumHA3, carry => carryHA3);

```

HA4: halfadder port map (A => sumHA3, B => carryHA3, sum => sumHA4, carry => carryHA4);

-- Final sum

Sum <= sumHA4;

end Behavioral;

-----half adder

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

entity halfadder is

Port (A : in STD_LOGIC_VECTOR(3 downto 0);

B : in STD_LOGIC_VECTOR(3 downto 0);

sum : out STD_LOGIC_VECTOR(3 downto 0);

carry : out STD_LOGIC_VECTOR(3 downto 0));

end halfadder;

architecture Behavioral of halfadder is

begin

process(A, B)

begin

Sum <= (A xor B);

carry(0) <= (A(0) and B(0));

carry(1) <= (A(1) and B(1)) or (A(0) and B(0));

carry(2) <= (A(2) and B(2)) or (A(1) and B(1)) or (A(0) and B(0));

carry(3) <= (A(3) and B(3)) or (A(2) and B(2)) or (A(1) and B(1)) or (A(0) and B(0));

end process;

end Behavioral;

-----subtraction


```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity subt is

    Port ( A : in STD_LOGIC_VECTOR(3 downto 0);
          B : in STD_LOGIC_VECTOR(3 downto 0);
          diff : out STD_LOGIC_VECTOR(3 downto 0));

end subt;

```

```

architecture Behavioral of subt is

    signal B_not: STD_LOGIC_VECTOR(3 downto 0);

begin

    B_not <= not B + 0001;

    diff <= A + B_not;

end Behavioral;

```

----nand gate

-- Bitwise Logic Module

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity bitwise_nand is

    Port ( A : in STD_LOGIC_VECTOR(3 downto 0);
          B : in STD_LOGIC_VECTOR(3 downto 0);
          Result_nand : out STD_LOGIC_VECTOR(3 downto 0));

end bitwise_nand;

```

```

architecture Behavioral of bitwise_nand is

```

```

begin
    process (A, B)
    begin
        Result_nand <= A nand B;
    end process;
end Behavioral;

```

----comparison

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

```

entity comparison is

```

    Port ( A : in STD_LOGIC_VECTOR(3 downto 0);
          B : in STD_LOGIC_VECTOR(3 downto 0);
          comp : out STD_LOGIC_VECTOR(3 downto 0));
end comparison;

```

architecture Behavioral of comparison is

```

begin
    process(A, B)
    begin
        if A > B then
            comp <= A;
        else
            comp <= B;
        end if;
    end process;
end Behavioral;

```

----xor gate

```

library IEEE;

```

```

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.STD_LOGIC_ARITH.ALL;

use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity Bitwise_Logic is

    Port ( A : in STD_LOGIC_VECTOR(3 downto 0);
          B : in STD_LOGIC_VECTOR(3 downto 0);
          Result : out STD_LOGIC_VECTOR(3 downto 0));

end Bitwise_Logic;

```

architecture Behavioral of Bitwise_Logic is

```

begin

    process (A, B)

        begin

            Result <= A xor B;

        end process;

    end Behavioral;

```

-----rotation

```

library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

```

```

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

```

```

-- Uncomment the following library declaration if instantiating
-- any Xilinx leaf cells in this code.
--library UNISIM;

--use UNISIM.VComponents.all;

```

entity rotate is

```
Port ( A : in STD_LOGIC_VECTOR(3 downto 0);  
      B : in STD_LOGIC_VECTOR(3 downto 0);  
      resRo : out STD_LOGIC_VECTOR(3 downto 0));
```

end rotate;

architecture Behavioral of rotate is

```
signal new_res: STD_LOGIC_VECTOR(3 downto 0);  
  
begin
```

```
new_res(0) <= A(3);
```

```
new_res(1) <= A(2);
```

```
new_res(2) <= A(1);
```

```
new_res(3) <= A(0);
```

```
resRo <= new_res;
```

```
end Behavioral;
```

-----shifting Left

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

entity shiftLeft is

```
Port ( A : in STD_LOGIC_VECTOR(3 downto 0);  
      B : in STD_LOGIC_VECTOR(3 downto 0);  
      resL : out STD_LOGIC_VECTOR(3 downto 0));
```

end shiftLeft;

architecture Behavioral of shiftLeft is

```
signal new_res: STD_LOGIC_VECTOR(3 downto 0);  
  
begin
```

```

new_res(0) <= A(1);
new_res(1) <= A(2);
new_res(2) <= A(3);
new_res(3) <= '1';
resL <= new_res;
end Behavioral;

```

-----shift Right

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
--use UNISIM.VComponents.all;

```

entity shiftRight is

```

    Port ( A : in STD_LOGIC_VECTOR(3 downto 0);
          B : in STD_LOGIC_VECTOR(3 downto 0);
          resR : out STD_LOGIC_VECTOR(3 downto 0));

```

end shiftRight;

architecture Behavioral of shiftRight is

signal new_res: STD_LOGIC_VECTOR(3 downto 0);

begin

```

new_res(0) <= A(1);
new_res(1) <= A(2);
new_res(2) <= A(3);
new_res(3) <= '1';
resR <= new_res;
end Behavioral;

```

----simulation sources

```
library IEEE;

use IEEE.STD_LOGIC_1164.ALL;

use IEEE.NUMERIC_STD.ALL;
```

```
entity sim is

end sim;
```

```
architecture Behavioral of sim is
```

```
    signal in1_test : std_logic_vector(3 downto 0) := (others => '0');
    signal in2_test : std_logic_vector(3 downto 0) := (others => '0');
    signal output_test : std_logic_vector(3 downto 0) := (others => '0');
    signal op_test : std_logic_vector(2 downto 0) := (others => '0');
```

```
begin
```

```
    DUT: entity work.mainmodule
```

```
        port map (
            in1 => in1_test,
            in2 => in2_test,
            output => output_test,
            op => op_test
        );
```

```
process
```

```
begin
```

```
    for i in 0 to 7 loop
        op_test <= std_logic_vector(to_unsigned(i, op_test'length));

        for a in 0 to 15 loop
            in1_test <= std_logic_vector(to_unsigned(a, in1_test'length));

            for b in 0 to 15 loop
                in2_test <= std_logic_vector(to_unsigned(b, in2_test'length));

                wait for 0.5ns;
            end loop;
        end loop;
    end loop;
```

```

        wait for 0.5ns;

    end loop;

    wait for 0.5ns;

    end loop;

end process;

end Behavioral;

```

----constraint

```

set_property PACKAGE_PIN V17 [get_ports {in2[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[0]}]
set_property PACKAGE_PIN V16 [get_ports {in2[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[1]}]
set_property PACKAGE_PIN W16 [get_ports {in2[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[2]}]
set_property PACKAGE_PIN W17 [get_ports {in2[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in2[3]}]
set_property PACKAGE_PIN W15 [get_ports {in1[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in1[0]}]
set_property PACKAGE_PIN V15 [get_ports {in1[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in1[1]}]
set_property PACKAGE_PIN W14 [get_ports {in1[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in1[2]}]
set_property PACKAGE_PIN W13 [get_ports {in1[3]}]
set_property IOSTANDARD LVCMOS33 [get_ports {in1[3]}]
set_property PACKAGE_PIN R2 [get_ports {op[2]}]
set_property IOSTANDARD LVCMOS33 [get_ports {op[2]}]
set_property PACKAGE_PIN T1 [get_ports {op[1]}]
set_property IOSTANDARD LVCMOS33 [get_ports {op[1]}]
set_property PACKAGE_PIN U1 [get_ports {op[0]}]
set_property IOSTANDARD LVCMOS33 [get_ports {op[0]}]

```

LEDs

set_property PACKAGE_PIN U16 [get_ports {output[0]}]

set_property IOSTANDARD LVCMOS33 [get_ports {output[0]}]

set_property PACKAGE_PIN E19 [get_ports {output[1]}]

set_property IOSTANDARD LVCMOS33 [get_ports {output[1]}]

set_property PACKAGE_PIN U19 [get_ports {output[2]}]

set_property IOSTANDARD LVCMOS33 [get_ports {output[2]}]

set_property PACKAGE_PIN V19 [get_ports {output[3]}]

set_property IOSTANDARD LVCMOS33 [get_ports {output[3]}]